

# EEE3088F RMTDIC001 Demo Notes

## FOR THE STM32

PA0-> LEFT ->LED7

PA1-> MIDDLE ->LED6

PA2-> RIGHT ->LED5

**DON'T FORGET TO COMMON GROUND STM, SENSOR AND POWER SUPPLY**

## System Interface Input

Table 1: System Interface Table **Sensor Board Input**


Origin	Destination	Use
3V3 Supply	Pin 2(Sensor Board)	Power
GND Supply	Pin 3(Sensor Board)	Power
GND Supply	STM Ground Pin	Power
3V3 Supply	Pin 10(Sensor Board)	Input Power
3V3 Supply	Pin 22(Sensor Board)	Input Power
3V3 Supply	Pin 20(Sensor Board)	Input Power

## System Interface Output

Table 2: System Interface Table **Sensor Board Output**


Origin	Destination	Use
Pin 5(Sensor Board)	PA1 STM	Front sense
Pin 7(Sensor Board)	PA2 STM	Right Sense
Pin 11(Sensor Board)	PA0 STM	Left Sense

## Connectors

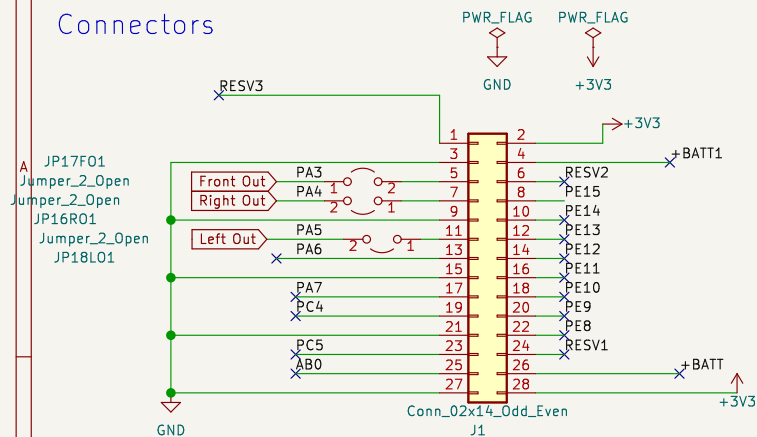


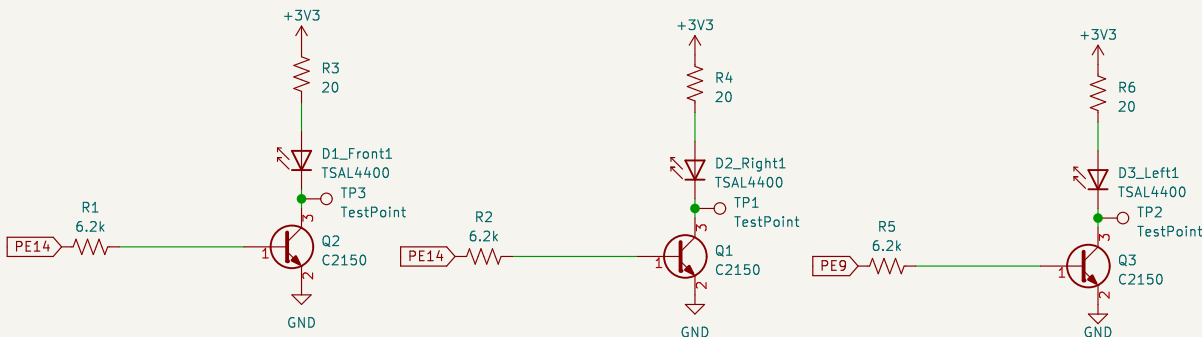
## IR Emmitters

The Emmitters+ Photodiodes complete the sesnor circuit  
The IR Emmitters emmit light at 940nm wavelength  
Optimal and exactly matched with the photodiode sesnitivity



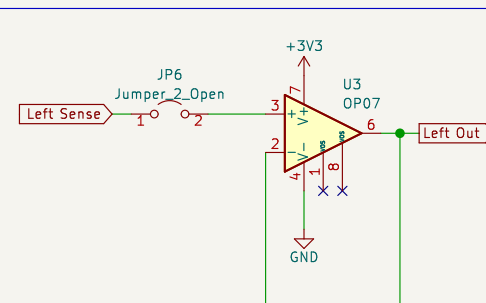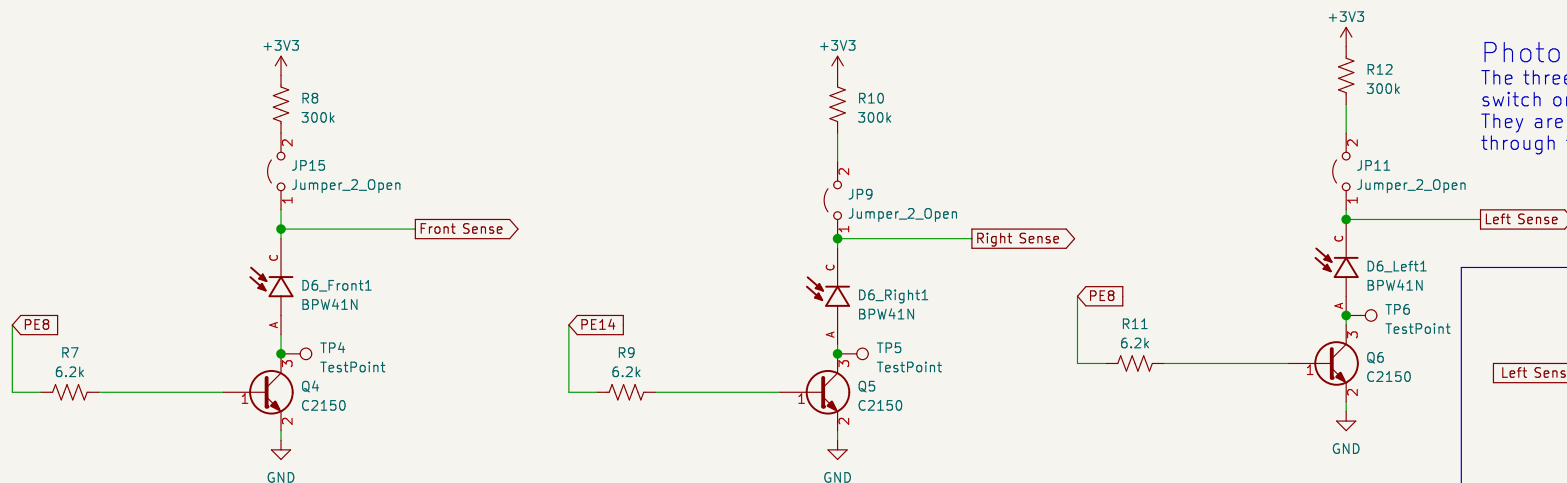
## Photo diodes

The three photodiodes for Front, Left and Right  
switch on and off to save power  
They are in sync with the IR Emmitters  
through the BJTs.



## Sensor Outputs

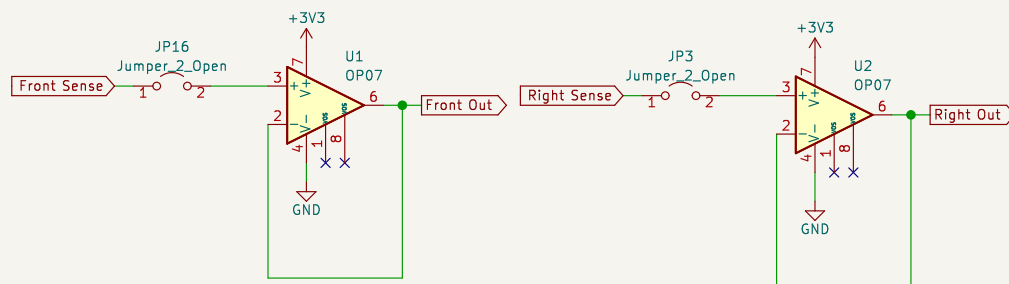

Ramotlou Dichochi  
RMTDIC001  
EEE3088F

University of Cape Town

Sheet:

File: MicroMouse Sensor .kicad\_sch

**Title: Micro Mouse Sensor**

Size: A4 Date: 2024-05-10

KiCad E.D.A. kicad (7.0.0-0)

Rev: v5.0

Id: 1/1